



Well bright sparks, you know that electricity always travels in a path and that to operate, a circuit must be complete. Trace the path from the switches below to see

